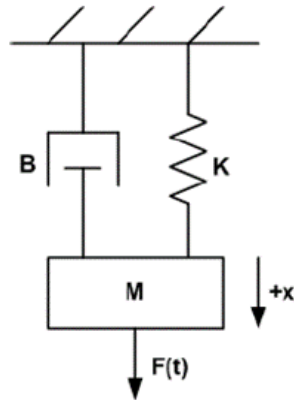


Tutorial 1


Mechanical Systems (Translational)

**Example:** Write the mathematical equation for the following mechanical system



**Answer:**

Free body diagram:

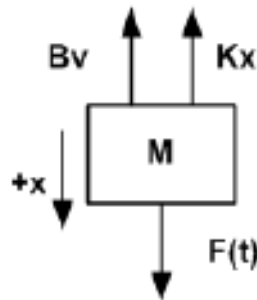


Math model:

$$\begin{aligned}\sum F_y &= Ma \\ -Bv - Kx + F &= Ma \\ a &= \frac{1}{M}(-Bv - Kx + F) \\ \text{Let } a &= \ddot{x}, v = \dot{x} \\ \ddot{x} &= \frac{1}{M}(-B\dot{x} - Kx + F)\end{aligned}$$

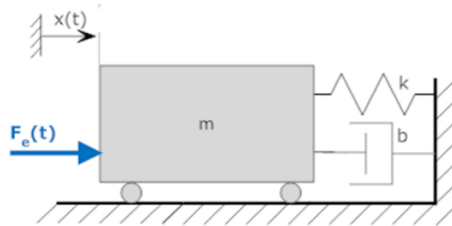**Example:** (Mass spring damper from Lecture 2)

Write the mathematical equation for the following mechanical system, where the input is the external force  $F_e$  and the output is position  $x(t)$ .



**Answer:**

Free body diagram:



Math model:

$$\sum_{all} F = 0$$

$$F_e(t) - ma(t) - bv(t) - kx(t) = 0$$

or

$$m \frac{d^2 x(t)}{dt^2} + b \frac{dx(t)}{dt} + kx(t) = F_e(t)$$

Or dot notation

$$m\ddot{x}(t) + b\dot{x}(t) + kx(t) = F_e(t)$$

**Remark:**


This equation is in our standard form (input-output notation):

Left hand side: system outputs (the unknown variables)

right hand side: system inputs (the known variables)

**Exercise:**

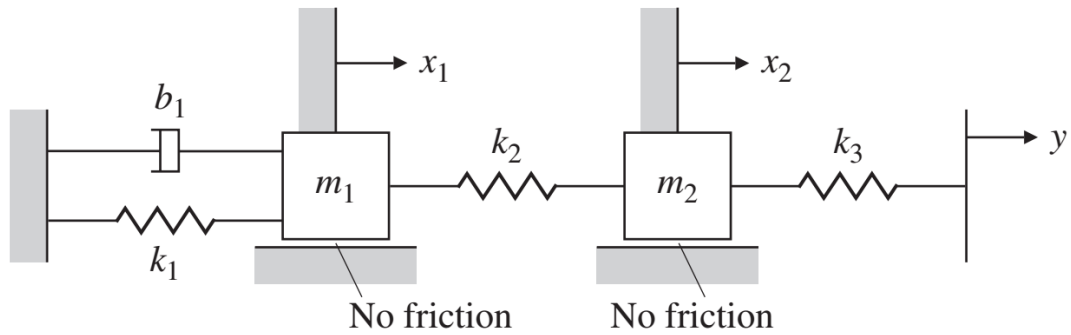**Q1)** Write the differential equations for the mechanical systems shown below. Assume that there are nonzero initial conditions for both masses and there is no input.



## Electrical systems

### Notes:

**Kirchhoff's voltage law:** *the algebraic sum of all voltages taken around any closed path in a circuit is zero.*

$$\sum_j v_j = 0$$

where  $v_j$  denotes the voltage across the  $j_{th}$  element in the loop


**Kirchhoff's current law:** *the algebraic sum of the currents at **any junction** is zero.*

$$\sum_j i_j = 0$$

where  $i_j$  denotes the current at the  $j_{th}$  node.
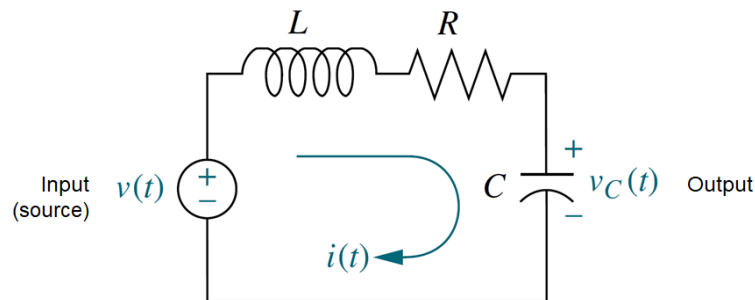
### Example:

Find the differential equation relating the capacitor voltage  $v_c(t)$  (output voltage), to the input voltage,  $v(t)$



### Answer:

- Summing the voltages around the loop, assuming zero initial conditions, yields the integral-differential equation:

$$v_{inductor} + v_{resistor} + v_{capacitor} = v_{in}$$

$$L \frac{di(t)}{dt} + i(t)R + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$

- Changing variables from current to charge using

$$i = \frac{dq}{dt}$$

(see Table 1 in lecture notes) yields:

$$L \frac{d^2 q(t)}{dt^2} + R \frac{dq(t)}{dt} + \frac{1}{C} q(t) = v(t)$$

- Changing variables from voltage to charge using

$$q = C v_c$$

(see Table 1 in lecture notes) yields:

$$LC \frac{d^2 v_c(t)}{dt^2} + RC \frac{dv_c(t)}{dt} + v_c(t) = v(t)$$


Where  $v(t)$  is the input voltage (source)

and  $v_c(t)$  is the output voltage

**Exercises:**

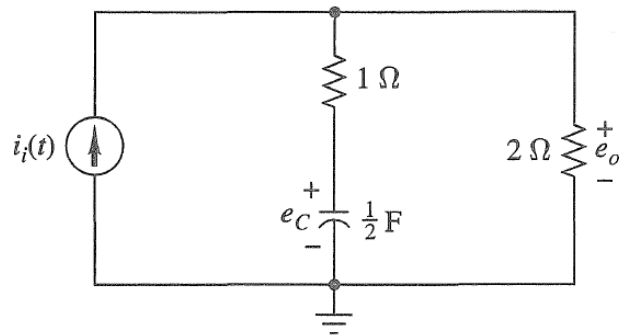**Q1)** Find the input-output differential equation relating the output voltage  $e_o(t)$ , to the input current,  $i_i(t)$  for the following circuit

*Remark: change of notation as compared to lecture notes. instead of voltage  $v$  here voltage is represented by  $e$*



**Q2)** Find the input-output differential equation relating the output voltage  $e_o(t)$ , to the input voltage,  $e_i(t)$  for the following circuit

*Remark: change of notation as compared to lecture notes. instead of voltage  $v$  here voltage is represented by  $e$*

