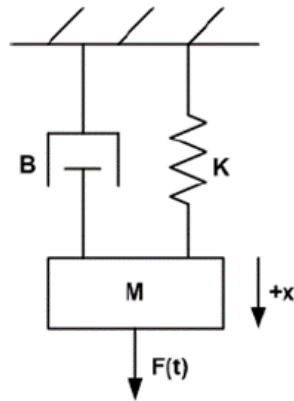


## ENG2009 – Modelling of Engineering Systems

### Tutorial 1


#### Mechanical Systems (Translational)

**Example:** Write the mathematical equation for the following mechanical system



**Answer:**

Free body diagram:

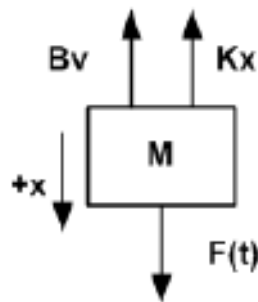


Math model:

$$\begin{aligned}\sum F_y &= Ma \\ -Bv - Kx + F &= Ma \\ a &= \frac{1}{M}(-Bv - Kx + F) \\ \text{Let } a &= \ddot{x}, v = \dot{x} \\ \ddot{x} &= \frac{1}{M}(-B\dot{x} - Kx + F)\end{aligned}$$

**Example:** (Mass spring damper from Lecture 2)

Write the mathematical equation for the following mechanical system, where the input is the external force  $F_e$  and the output is position  $x(t)$ .

(Mass spring damper from Lecture 2)

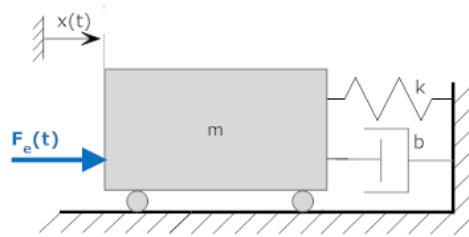

**Answer:**

Free body diagram:



Math model:

$$\sum_{all} F = 0$$

$$F_e(t) - ma(t) - bv(t) - kx(t) = 0$$

or

$$m \frac{d^2 x(t)}{dt^2} + b \frac{dx(t)}{dt} + kx(t) = F_e(t)$$

Or dot notation

$$m\ddot{x}(t) + b\dot{x}(t) + kx(t) = F_e(t)$$

**Remark:**


This equation is in our standard form (input-output notation):

Left hand side: system outputs (the unknown variables)

right hand side: system inputs (the known variables)


**Excercise:**

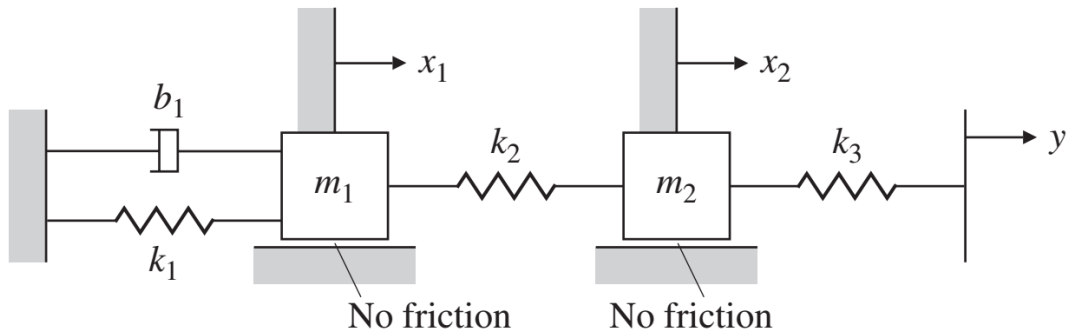**Q1)** Write the differential equations for the mechanical systems shown below. Assume that there are nonzero initial conditions for both masses and there is no input.



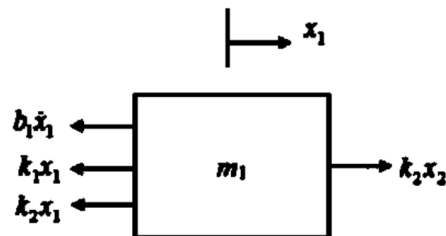**Q1) Answer:**

Draw the free body diagram of mass  $m_1$ .




Write the differential equation describing the system.

$$m_1 \ddot{x}_1 = -b_1 \dot{x}_1 - k_1 x_1 - k_2 x_1 + k_2 x_2$$

$$m_1 \ddot{x}_1 + b_1 \dot{x}_1 + k_1 x_1 + k_2 (x_1 - x_2) = 0$$

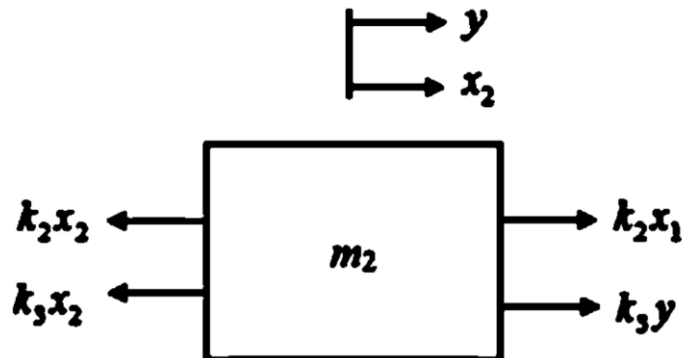Draw the free body diagram of mass  $m_2$ .



Write the differential equation describing the system.


$$m_2 \ddot{x}_2 = -k_2 x_2 - k_3 x_2 + k_2 x_1 + k_3 y$$

$$m_2 \ddot{x}_2 + k_2 (x_2 - x_1) + k_3 (x_2 - y) = 0$$


Thus, the differential equations describing the system are,

$$\boxed{\begin{aligned} m_1 \ddot{x}_1 + b_1 \dot{x}_1 + k_1 x_1 + k_2 (x_1 - x_2) &= 0 \\ m_2 \ddot{x}_2 + k_2 (x_2 - x_1) + k_3 (x_2 - y) &= 0 \end{aligned}}$$

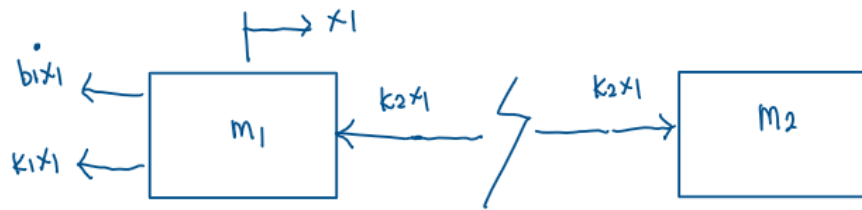case ①  $x_1 \neq 0$ ,  $x_2 = 0$ ,  $y = 0$   
FBD




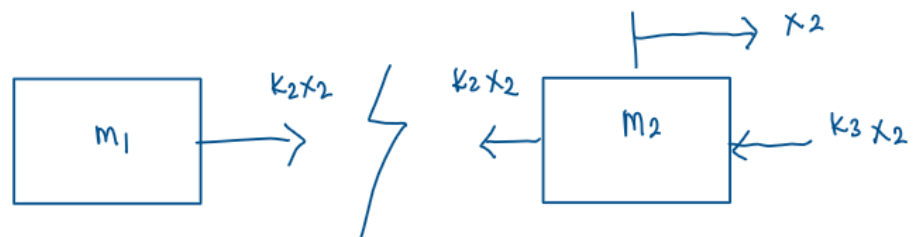
case ②  $x_1 = 0$ ,  $x_2 \neq 0$ ,  $y = 0$



case ③  $x_1 = 0$ ,  $x_2 = 0$ ,  $y \neq 0$



superposition

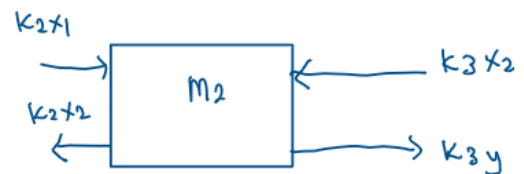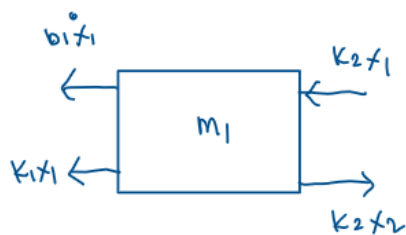

## Electrical systems

### Notes:

**Kirchhoff's voltage law:** *the algebraic sum of all voltages taken around any closed path in a circuit is zero.*

$$\sum_j v_j = 0$$

where  $v_j$  denotes the voltage across the  $j_{th}$  element in the loop


**Kirchhoff's current law:** *the algebraic sum of the currents at **any junction** is zero.*

$$\sum_j i_j = 0$$

where  $i_j$  denotes the current at the  $j_{th}$  node.
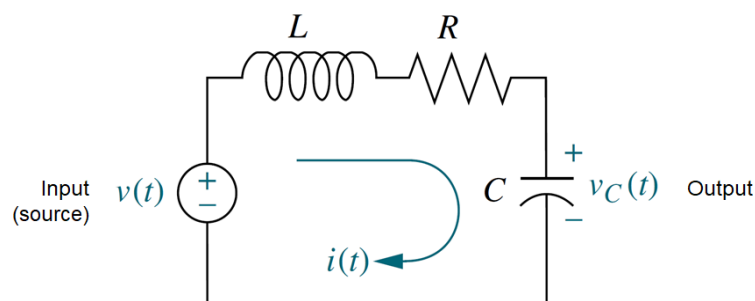
### Example:

Find the differential equation relating the capacitor voltage  $v_c(t)$  (output voltage), to the input voltage,  $v(t)$



### Answer:

- Summing the voltages around the loop, assuming zero initial conditions, yields the integral-differential equation:

$$v_{inductor} + v_{resistor} + v_{capacitor} = v_{in}$$

$$L \frac{di(t)}{dt} + i(t)R + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$

- Changing variables from current to charge using

$$i = \frac{dq}{dt}$$

(see Table 1 in lecture notes) yields:

$$L \frac{d^2 q(t)}{dt^2} + R \frac{dq(t)}{dt} + \frac{1}{C} q(t) = v(t)$$

- Changing variables from voltage to charge using

$$q = C v_c$$

(see Table 1 in lecture notes) yields:


$$LC \frac{d^2 v_c(t)}{dt^2} + RC \frac{dv_c(t)}{dt} + v_c(t) = v(t)$$

Where  $v(t)$  is the input voltage (source)

and  $v_c(t)$  is the output voltage

### Exercises:

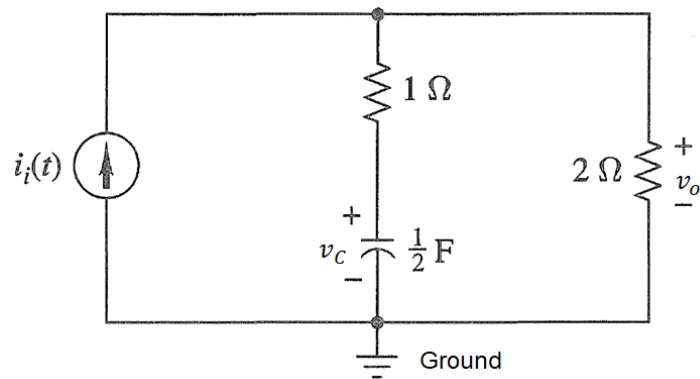
**Q1)** Find the input-output differential equation relating the output voltage  $v_o(t)$ , to the input current,  $i_i(t)$  for the following circuit



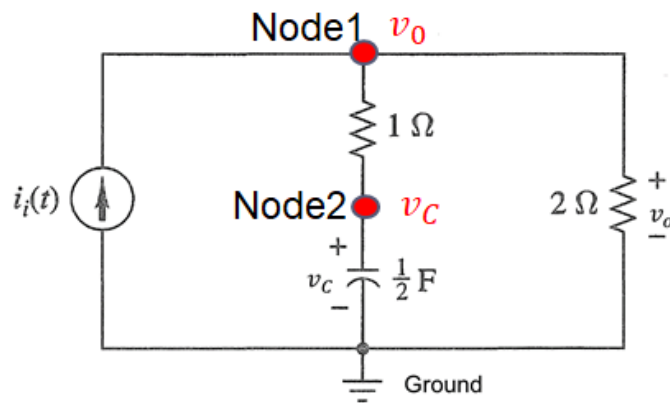**Answer:**


Strategy:

- Input: current  $i_i(t)$
- Output: the  $2\ \Omega$  resistor voltage  $v_o(t)$
- The node voltage with respect to ground at the top of the node is  $v_o$
- The node voltage with respect to ground at the top of the capacitor is  $v_c$
- Two simultaneous equations
- Use Kirchhoff's current law



Solution:

Node 1

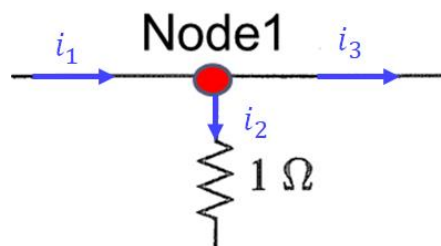

- Current law
- $i_1 = i_i$
- $i_2 = \frac{v_R}{R} = \frac{v_o - v_c}{1}$


- $i_3 = \frac{v_o}{R} = \frac{v_o}{2}$

Therefore at Node 1

$$i_1 = i_2 + i_3$$

$$i_i(t) = (v_o - v_c) + \frac{1}{2} v_o \quad (A)$$

Node 2

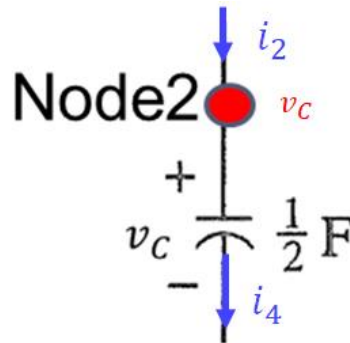

- Current law
- $i_2 = \frac{v_R}{R} = \frac{v_o - v_c}{1}$  (as before)
- $i_4 = C \frac{dv_c}{dt} = \frac{1}{2} \frac{dv_c}{dt}$

Therefore at Node 2

$$i_2 = i_4$$

$$(v_o - v_c) = \frac{1}{2} \frac{dv_c}{dt} \quad (B)$$

Overall equations, after rearranging both equation (A) and (B), to yield:

$$-i_i(t) + (v_o - v_c) + \frac{1}{2} v_o = 0 \quad (A)$$

$$\frac{1}{2} \frac{dv_c}{dt} + (v_c - v_o) = 0 \quad (B)$$

From (A),

$$v_c = \frac{3}{2} v_o - i_i$$

Sub into (B) to yield


$$\frac{3}{4} \frac{dv_o}{dt} + \frac{1}{2} v_o = \frac{1}{2} \frac{di_i}{dt} + i_i$$

which is the differential equation relating the

output voltage  $v_o(t)$ ,  
to the input current  $i_i(t)$




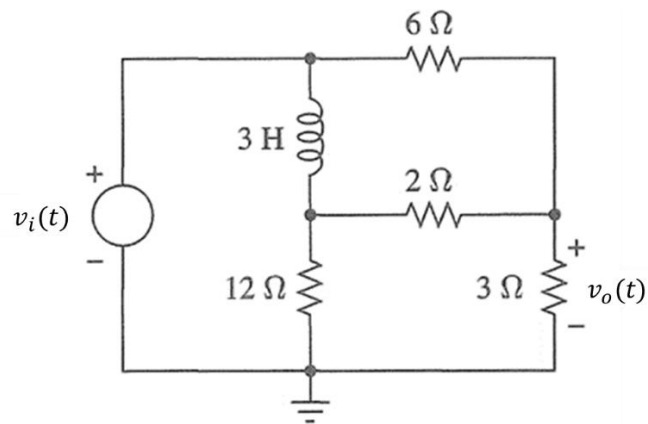**Q2)** Find the input-output differential equation relating the output voltage  $v_o(t)$ , to the input voltage,  $v_i(t)$  for the following circuit




**Answer:**

Define node A and node O

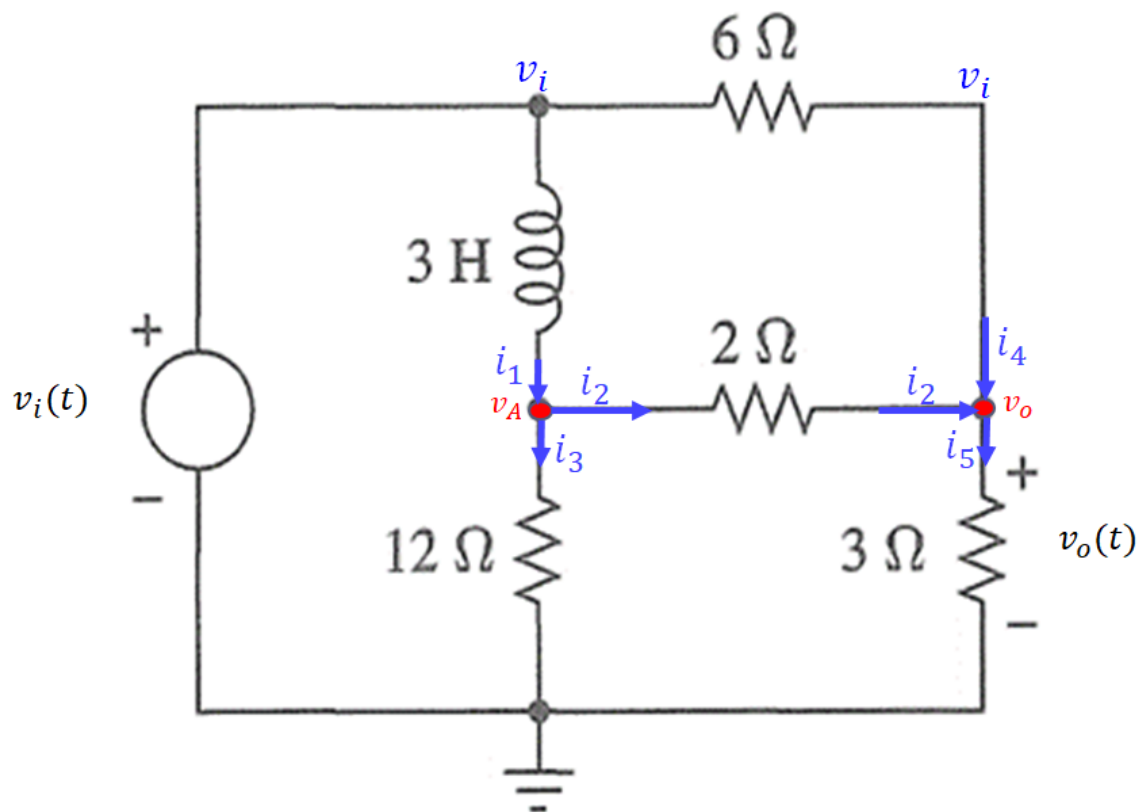

### Node A

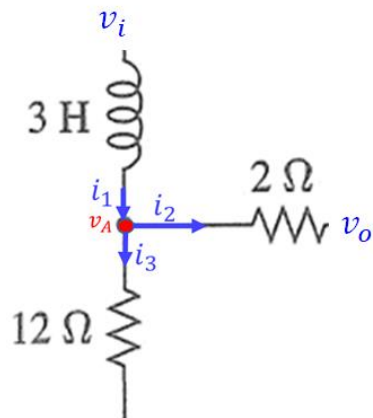


- Write current law at Node A
- $i_1 = \frac{1}{L} \int (v_i - v_A) d\tau = \frac{1}{3} \int (v_i - v_A) d\tau$
- $i_2 = \frac{v_A - v_o}{R} = \frac{v_A - v_o}{2}$
- $i_3 = \frac{v_A}{R} = \frac{v_A}{12}$

Therefore at Node A

$$\frac{1}{L} \int (v_i - v_A) d\tau = \frac{v_A - v_o}{2} + \frac{v_A}{12}$$

### Node O

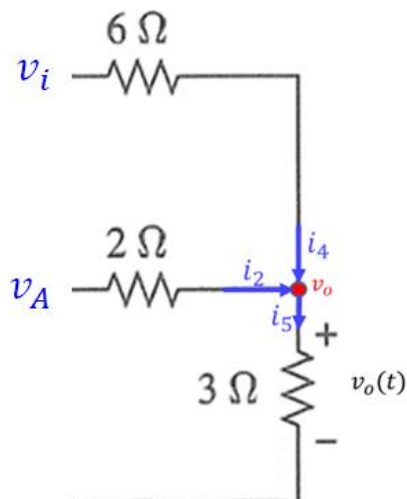

- Write current law at Node O
- $i_2 = \frac{v_A - v_o}{R} = \frac{v_A - v_o}{2}$  (as before)
- $i_4 = \frac{v_i - v_o}{R} = \frac{v_i - v_o}{6}$
- $i_5 = \frac{v_o}{R} = \frac{v_o}{3}$
- 

Therefore at Node O

$$\frac{v_o}{3} = \frac{v_A - v_o}{2} + \frac{v_i - v_o}{6}$$

Overall

$$\frac{1}{3} \int (v_i - v_A) d\tau = \frac{v_A - v_o}{2} + \frac{v_A}{12} \quad (\text{A})$$

$$\frac{v_o}{3} = \frac{v_A - v_o}{2} + \frac{v_i - v_o}{6} \quad (\text{B})$$

Differentiating (A) and simplify both (A) and (B) to yield

$$7\dot{v}_A + 4v_A - 6\dot{v}_o = 4v_i \quad (\text{A})$$

$$-3\dot{v}_A + 6\dot{v}_o = \dot{v}_i \quad (\text{B})$$

From (B)

$$v_A = 2v_o - \frac{1}{3}v_i$$

Sub into (A) to yield

$$\dot{v}_o + v_o = \frac{7}{24} \dot{v}_i + \frac{2}{3} v_i$$

which is the differential equation relating the

**output voltage  $v_o(t)$ ,**

to the **input voltage  $v_i(t)$**

given  $\frac{1}{3} \int (v_i - v_A) dx = \frac{v_A - v_0}{2} + \frac{v_A}{12} \quad (A)$

$$\frac{v_0}{3} = \frac{v_A - v_0}{2} + \frac{v_i - v_0}{6} \quad (B)$$

from (A), differentiate:

$$\frac{d}{dx} \left( \frac{4}{3} \int (v_i - v_A) dx \right) = \left( \frac{6}{2} (v_A - v_0) + v_A \right) \frac{d}{dx}$$

$$4(v_i - v_A) = 6(\dot{v}_A - \dot{v}_0) + \dot{v}_A$$

$$4v_i - 4v_A = 7\dot{v}_A - 6\dot{v}_0$$

rearrange

$$7\dot{v}_A - 6\dot{v}_0 + 4v_A = 4v_i \quad (A^*)$$

from (B) rearrange

$$2\frac{6}{3}v_0 = \frac{6}{2}(v_A - v_0) + (v_i - v_0)$$

$$6v_0 - 3v_A = v_i \quad (B^*)$$

rearrange

$$v_A = \frac{1}{3}(6v_0 - v_i)$$

$$v_A = 2v_0 - \frac{1}{3}v_i \quad \text{Sub into } (A^*)$$

$$7 \frac{1}{\hbar} (2v_0 - \frac{1}{3} \dot{v}_0) - 6 \dot{v}_0 + 4 (2v_0 - \frac{1}{3} \dot{v}_0) = 4 \dot{v}_0$$

$$14 \dot{v}_0 - \frac{7}{3} \dot{v}_0 - 6 \dot{v}_0 + 8 v_0 - \frac{4}{3} \dot{v}_0 = 4 \dot{v}_0$$

$$8 \dot{v}_0 - \frac{7}{3} \dot{v}_0 + 8 v_0 = (4 + \frac{4}{3}) \dot{v}_0$$

$$8 (\dot{v}_0 + v_0) = \frac{7}{3} \dot{v}_0 + (12 + \frac{4}{3}) v_0$$

$$(\dot{v}_0 + v_0) = \frac{7}{24} \dot{v}_0 + (\frac{16}{3}) (\frac{1}{8}) v_0$$

$$(\dot{v}_0 + v_0) = \frac{7}{24} \dot{v}_0 + \frac{2}{3} v_0 \quad \#$$


---

### EXTRA: Python simulation of a mass-spring-damper system

```
#import numpy, integrate and pyplot
import numpy as np
from scipy import integrate
from matplotlib import pyplot as plt

#sim data
m=2 #mass of the oscillator
b=0.1 #damper of the oscillator
k=1 #stiffness of the oscillator
omega = (k/m)**0.5 #angular frequency of the oscillator
T=2*np.pi/omega #period of the oscillator

#create 1000 uniformly distributed points in the interval [0,10T]
t = np.linspace(0,10*T,1000)

#lambda returning the force
force = lambda t: np.sin(1.0*omega*t)
Inputs=np.sin(1.0*omega*t)

#lambda with the RHS of the equation, it evaluates the force and
returns a list
f = lambda X,t: [X[1],1/m*(force(t)-k*X[0]-b*X[1])]

#solve equation using odeint, now the values of X for t=0 are given
by a list
Xodeint = integrate.odeint(f,[0,0],t)

plt.plot(t,Inputs)
plt.title('Force (input)')
plt.xlabel('$t$')
plt.ylabel('$input$')
plt.show()

#plot displacements from both solutions (first column of each
solution)
plt.plot(t,Xodeint[:,0])
plt.legend(['Odeint'])
plt.title('Displacements')
plt.xlabel('$t$')
plt.ylabel('$x$')
plt.show()

#plot velocities from both solutions (first column of each solution)
plt.plot(t,Xodeint[:,1])
plt.legend(['Odeint'])
plt.title('Velocities')
plt.xlabel('$t$')
plt.ylabel('$\dot{x}$')
plt.show()

#Save data
np.savetxt('t.txt',t)
np.savetxt('x.txt',Xodeint[:,0])
```

## Simulation results

